

clk Botones sw rst clk div 4 Mux FSM Read_mode leds [6:4] Contador leds [3:0] LEDs 16 16 ALU 7 16 Registros 32x16 bits 16 **LFSR** Mux В 7-segment Display

Diagrama de Nivel 2 de la Mini Unidad de Cálculo

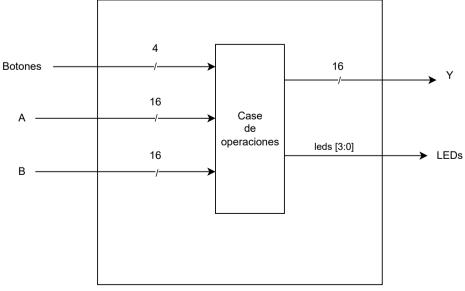


Diagrama de Nivel 3 de la ALU